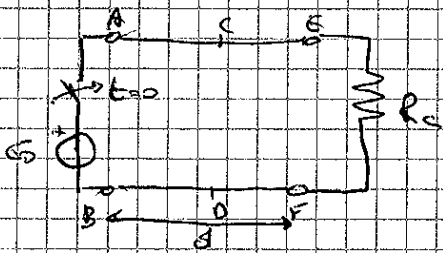


# Esercizio

$\omega = \frac{1}{\sqrt{LC}}$        $Z_{00} = \sqrt{\frac{L}{C}}$

$\Gamma_c = \frac{R_c - Z_{00}}{R_c + Z_{00}}$   
 $\Gamma_g = \frac{R_g - Z_{00}}{R_g + Z_{00}}$

Linee rette perdite trasmissioni



$E_0 = 30 \text{ V}$        $R_c = 100 \Omega$        $R_g = 50 \Omega$        $\omega = 200 \frac{\text{m}}{\mu\text{s}}$

$d = 400 \text{ m}$

Dobbiamo trovare  $V$  e  $I$  per  $x = \frac{d}{2}$


per  $t = 2 \mu\text{s}$

$V_{AB} = E_0$        $V_E$   
 $V_{CF} = RI(x=d)$


$N^+ = Z_{00} I^+$       e       $N^- = -Z_{00} I^-$       definiamo       $t_0 = \frac{d}{\omega} = \frac{400 \text{ m}}{200 \frac{\text{m}}{\mu\text{s}}} = 2 \mu\text{s}$

$\Gamma_c = \frac{2-1}{2+1} = \frac{1}{3}$        $\Gamma_g = -1$

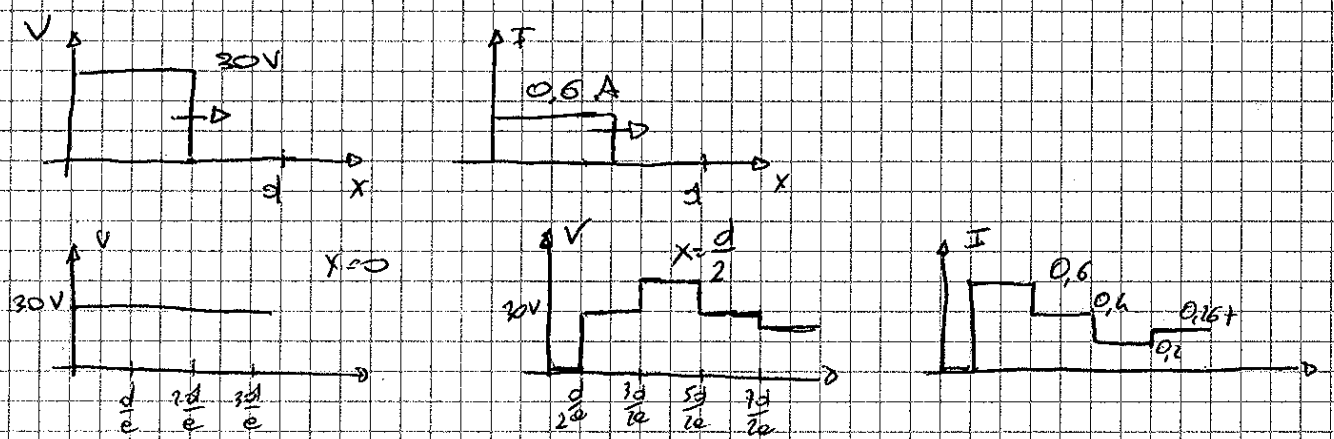$\odot \rightarrow \frac{d}{\omega}$        $N = N_0 + N^+$        $N^+ = E_0 = 30 \text{ V}$   
 $i = i_0 + i^+$        $i^+ = \frac{E_0}{Z_{00}} = 0,6 \text{ A}$




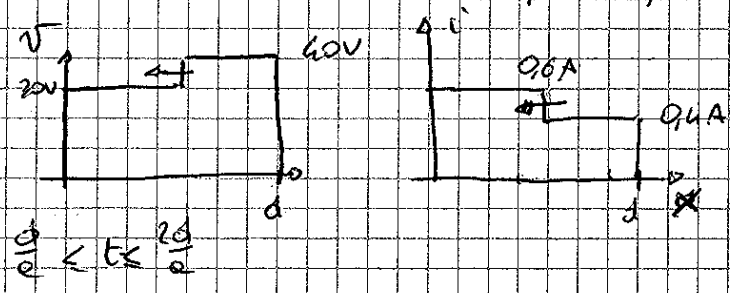
$\text{in } x = d \text{ e } t = \frac{d}{\omega}$   
 $N = E_0 + N_c^- = 10$        $N = \frac{1}{3} E_0 = 10 \text{ V}$   
 $i = 0,6 - \frac{N_c^-}{Z_{00}} = 0,4 \text{ A}$        $i_c^- = 0,2 \text{ A}$



in  $X=0$  e  $t = \frac{2d}{c}$


$V_3^+ = -V_2^- = -10V$

$i_3^+ = \frac{V_3^+}{Z_{00}} = -0,2A$

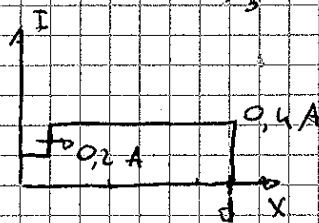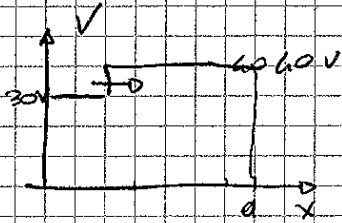


$V = V_1^+ + V_2^- + V_3^+ = 30V$   
 $i = i_1^+ + i_2^- + i_3^+ = 0,2A$

in  $X=d$  e  $t = \frac{3d}{2}$

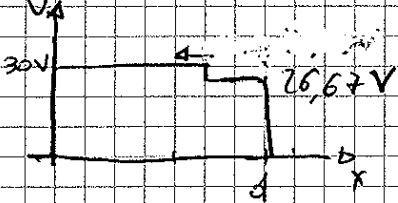


$V_4^- = \frac{1}{3} V_3^+ = -3,33V$   
 $i_4^- = -\frac{V_4^-}{Z_{00}} = +0,067$

$V = 26,67V$   
 $i = 0,267A$

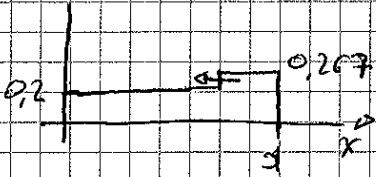

Esercizio 2

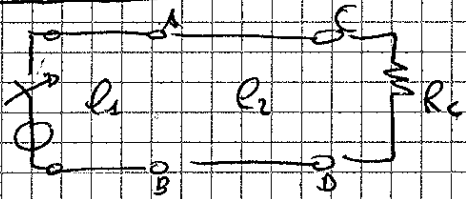

	a	c	d
linea 1	$150 \frac{\mu H}{m}$	$71 \frac{pF}{m}$	$10 km$
linea 2	$900 \frac{\mu H}{m}$	$100 \frac{pF}{m}$	$50 m$

$R_c = 50 \Omega$

$E_0 = 10 kV$

$V_{ab}(t) = ?$

$V_{cd}(t) = ?$

$0 \leq t \leq \frac{d_1}{c_1} + \frac{3d_2}{c_2}$

$c_1 = \frac{1}{\sqrt{\epsilon c}} = \frac{3005 m}{\mu s}$

$c_2 = \frac{1}{\sqrt{\epsilon c}} = \frac{150,7 m}{\mu s}$

$0 \leq t \leq 33,3 \mu s + 9,9 \mu s = 43,2 \mu s$

$Z_{001} = 468 \Omega$

$Z_{002} = 66,3$


$\Gamma_{cg} = -1$

$\Gamma_{AB1} = \frac{\frac{Z_{002} + R_c}{Z_{002}} + 1}{\frac{Z_{002} + R_c}{Z_{001}} + 1} = \frac{\frac{66,3 + 50}{468} + 1}{\frac{66,3 + 50}{468} + 1} = \frac{1,754}{1,146} = -0,75$

Linea 1

$V_1^+ = 10 kV$   
 $i_1^+ = 21,36 A$

$V_2^- = \Gamma_{AB1} \cdot V_1^+ = -7500 V$   
 $i_2^- = -\frac{V_2^-}{Z_{001}} = 16,02 A$

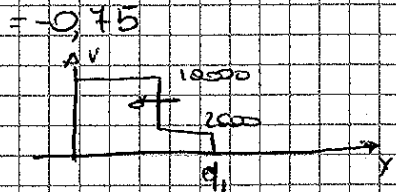

Linea 2

$V_{AB} = 2500 V$



$\Gamma_{AB2} = \frac{\frac{Z_{001}}{Z_{002}} - 1}{\frac{Z_{001}}{Z_{002}} + 1} = \frac{6,0588}{8,0588} = 0,75$

$\Gamma_c = \frac{-0,2458}{1,754} = -0,14$

$$V_1^+ = 2500 \text{ V}$$

$$I_1^+ = \frac{2500}{Z_{01}} \text{ V} = 37,7 \text{ A}$$

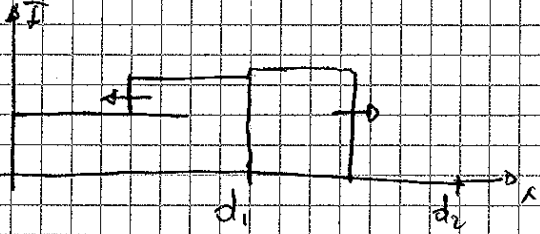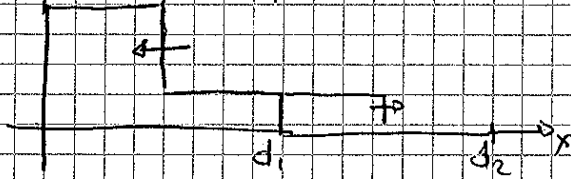
per ~~1~~  $\lambda$   $\rightarrow$   $\text{cabo}$



$$V_2^- = \Gamma_{102} V_1^+ = -350 \text{ V}$$


$$I_2^- = -\frac{V_2^-}{Z_{02}} = 5,28$$

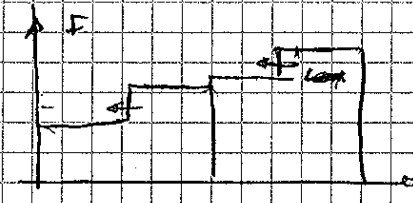$\lambda$   $\rightarrow$   $\text{cabo}$



$$V_3^+ = \Gamma_{102} V_2^- = -262,5 \text{ V}$$
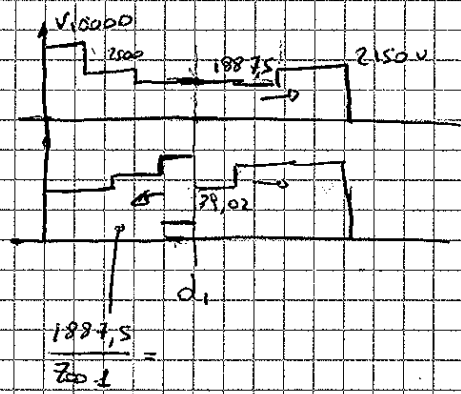
$$I_3^+ = \frac{V_3^+}{Z_{02}} = -3,96 \text{ A}$$



x